
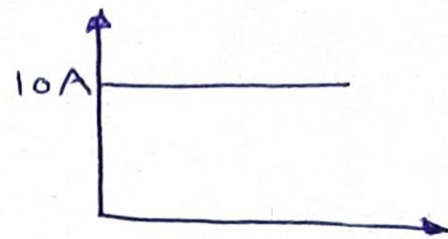


# Fundamental of Electrical Engineering

DC: Direct Current

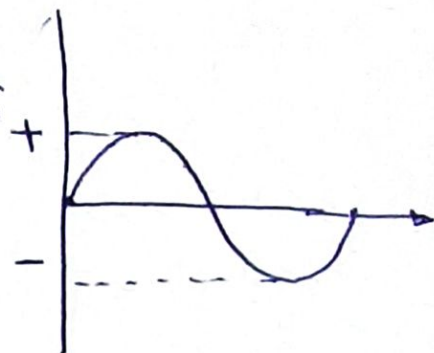


AC: Alternative Current




Voltage  $[V]$ : The potential difference between two points.

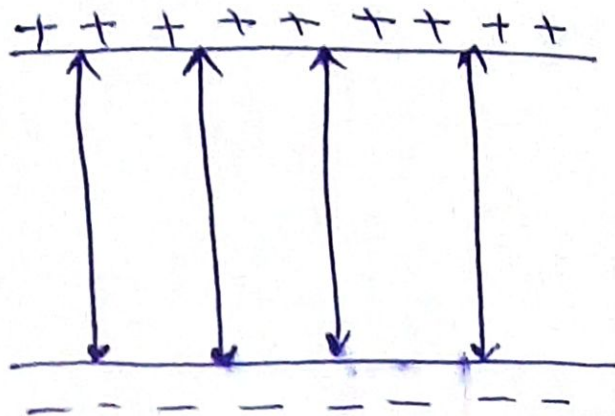
Current  $[I]$ : The rate of Charge moving in a certain metal.



Voltage Source

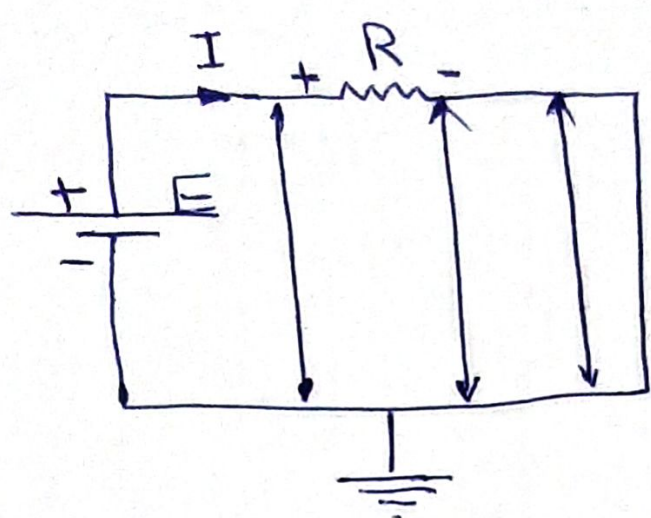

Current Source

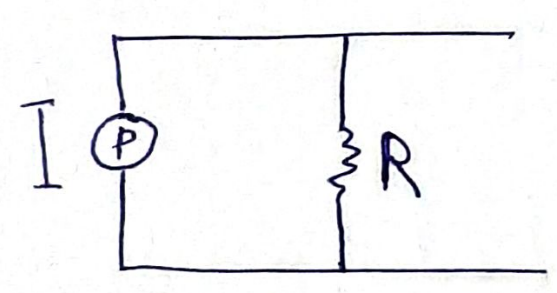


Ohm's Law

$$R = \frac{V}{I} , I = \frac{V}{R} , V = I \cdot R$$

$$R [\Omega] , V [V] , I [A]$$

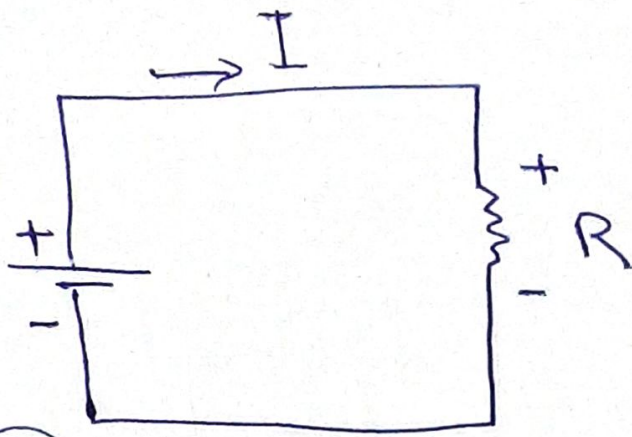$\downarrow$  ohm                       $\downarrow$  volt                       $\downarrow$  Amp





Power

$$P = V \cdot I$$

$$\therefore P = I^2 \cdot R$$


or

$$P = \frac{V^2}{R}$$


$$\therefore R = \frac{V}{I}$$

# (Kirchoff's law)


## 1) Kirchoff's Current law (KCL)

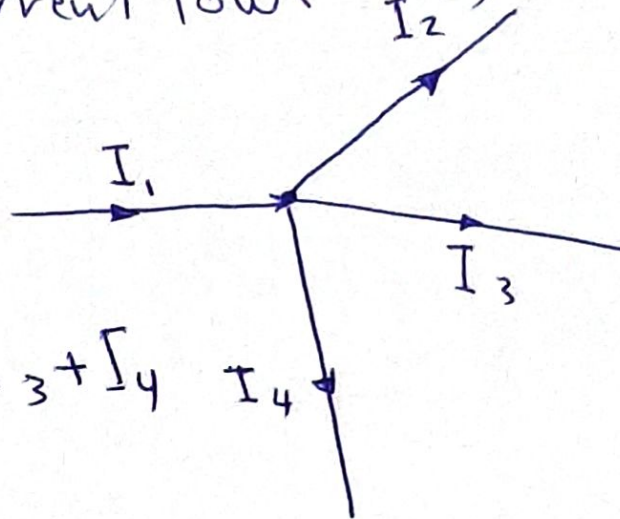

$$I_1 = I_2 + I_3 + I_4$$

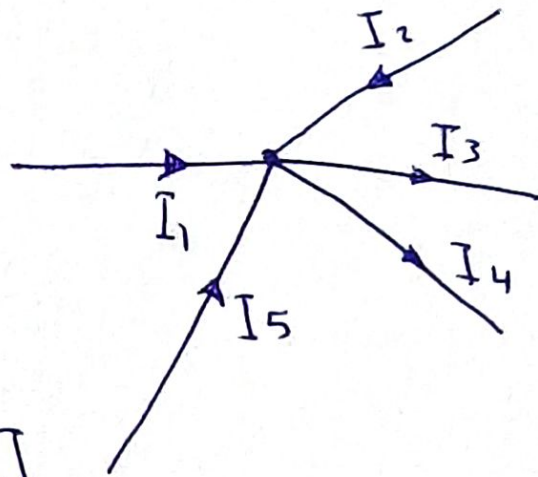


$$I_1 + I_2 + I_5 = I_3 + I_4$$

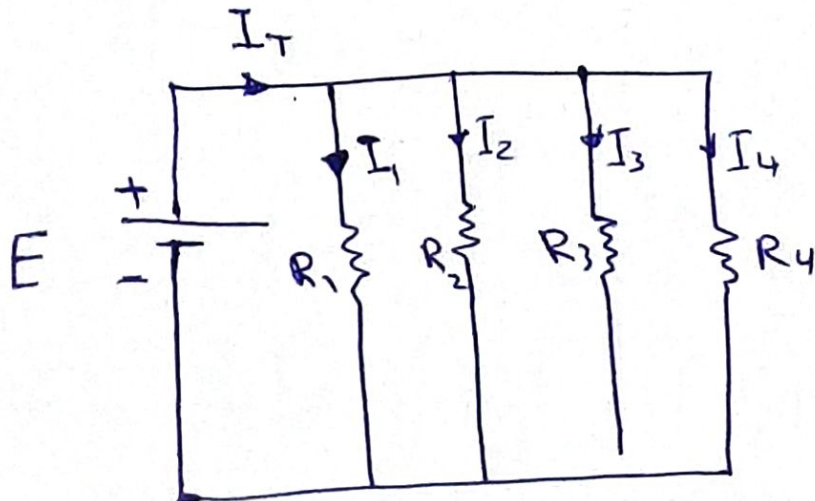

⇒ Parallel  
توازی




## (2) Kirchhoff's voltage law [KVL]

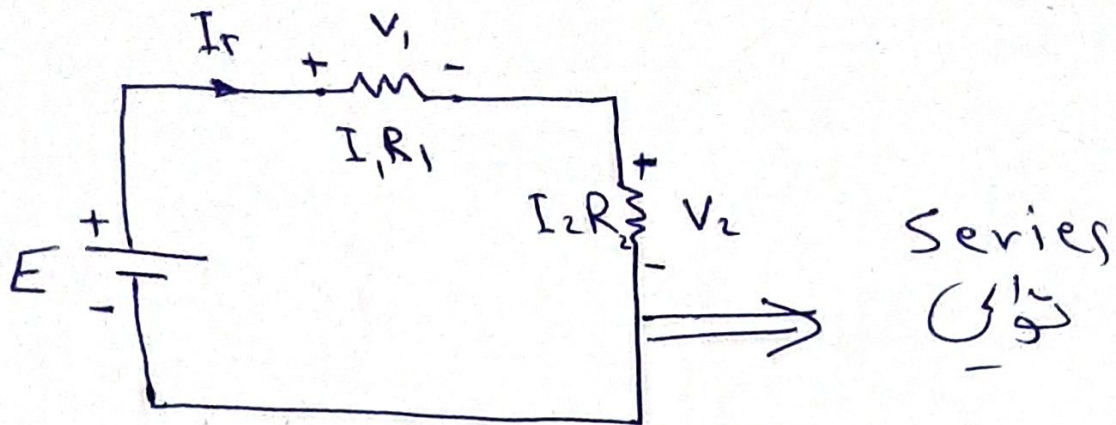


$$E = V_1 + V_2 \Rightarrow E - V_1 - V_2 = 0$$

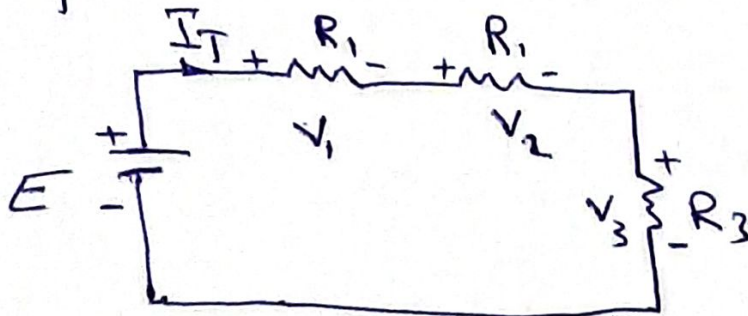\* عملہ / المقادیر على التوالي يتم جمعها لإيجاد مقادير كل واحد



$$R = \frac{V}{I} \Rightarrow I_T = \frac{E}{R_T} \quad R_T = R_1 + R_2 + R_3$$

Ex<sub>1</sub> for the Circuit Shown:

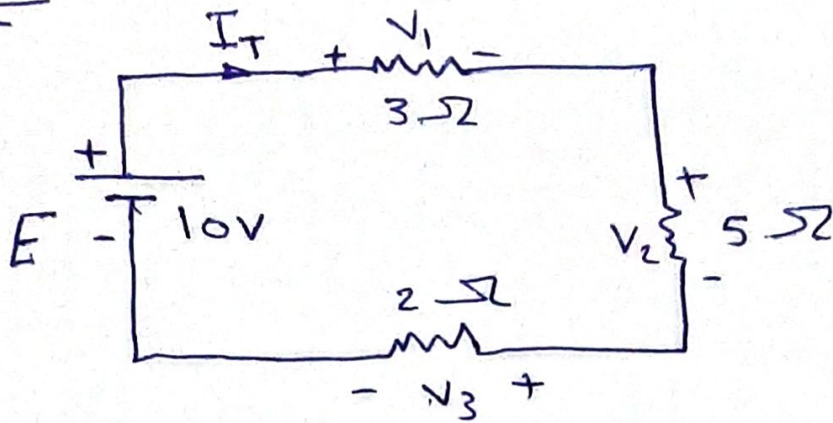

Find The voltage  $V_1, V_3$

Sol  $R_1 = \frac{V_1}{I_1}$  ,  $R_2 = \frac{V_2}{I_2}$  ,  $R_3 = \frac{V_3}{I_3}$

$$I_T = I_1 = I_2 = I_3$$

$$I_T = \frac{E}{R_T} \rightarrow 10V$$

$$R_T = R_1 + R_2 + R_3$$
$$= 3 + 5 + 2$$

$$R_T = 10$$

$$I_T = \frac{10}{10} = 1A$$

$$V_1 = I_T * R_1$$

$$V_1 = 1 * 3 = 3V$$

$$V_3 = 1 * 2 = 2V$$

(6)



4/24

# Voltage divider rule (VDR)

$$V_x = \frac{E \cdot R_x}{R_T}$$


Ex. Determine the voltages  $V_1$ ,  $V_2$  and  $V'$  for the Circuit Shown

$$V_1 = \frac{E \cdot R_1}{R_T}$$


$$V_1 = \frac{50 \times 3}{14} = 10.7 \text{ V}$$

$$V_2 = \frac{50 \times 5}{14} = 17.85 \text{ V}$$

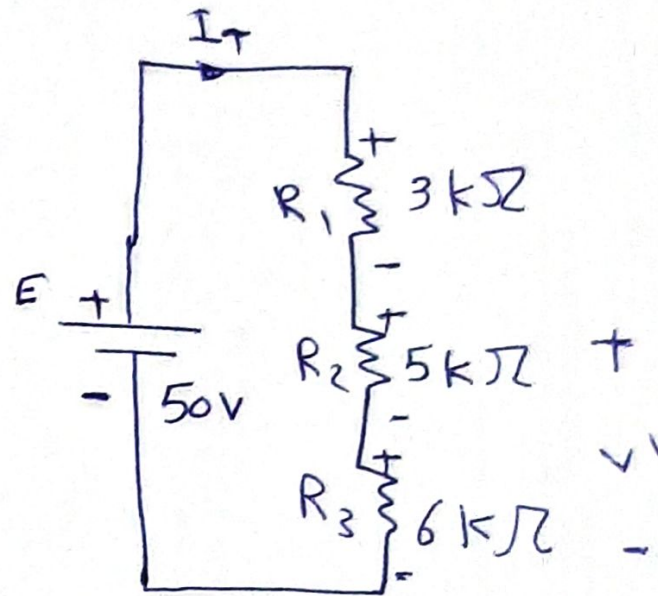
$$V' = \frac{E \cdot R'}{R_T} = \frac{50 \times 11}{14} = 39.28 \text{ V}$$




سلسلة / في حالة تفرع

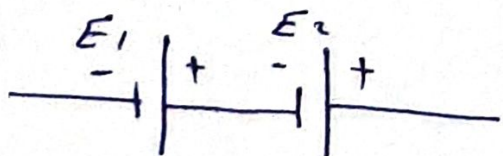

$$E_T = E_1 + E_2$$

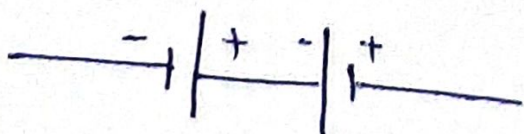


$$E_T = E_1 - E_2$$

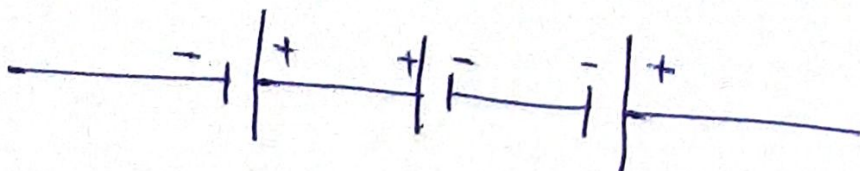

$$E_T = E_1 - E_2 + E_3$$

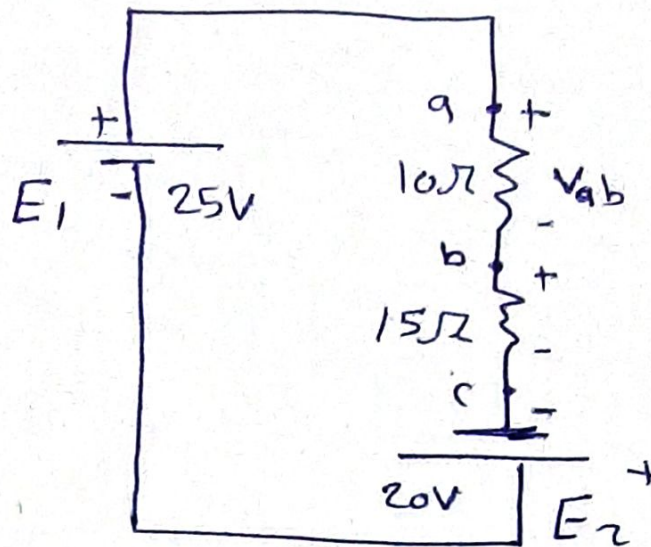(7)

EX Find  $V_{ab}$  and  $V_{ac}$  for the circuit shown



$$V_{ab} = ?$$

$$V_{ac} = ?$$

$$E_T = E_1 + E_2 = 45V$$

$$R_T = R_{ab} + R_{bc} = 25\Omega$$

$$V_{ab} = \frac{E_T \cdot R_{ab}}{R_T} = \frac{45 \cdot 10}{25} = 18V$$

$$V_{ac} = \frac{E_T \cdot R_{ac}}{R_T} = \frac{45 \cdot 25}{25} = 45V$$